

**JF-114**

January-2021

**B.C.A., Sem.-III**

**CC-201 : Computer Organization  
(New Course)**

[Max. Marks : 50

Time : 2 Hours]

- Instructions :**
- (1) All Questions in Section I carry equal marks.
  - (2) Attempt any TWO questions in Section I.
  - (3) Question 5 in Section II is COMPULSORY.

**Section - I**

1. (A) List the different types of Gate, explain all in detail with diagram and Truth Table. 10  
(B) List the different types of Flip-Flops. Explain JK Flip-flop and T Flip-flop in detail. 10
2. (A) Explain Bus Memory Transfer in detail with diagram. 10  
(B) Explain Binary Adder and Binary Adder Subtractor in detail. 10
3. (A) Explain Common Bus System in detail with diagram. 10  
(B) List the different types of Addressing Modes. Explain Immediate, Direct, Indirect and Register Indirect mode in detail. 10
4. (A) Explain I/O Bus System, Isolated and Memory-Mapped I/O in detail. 10  
(B) Explain Cache Memory, Main Memory and Associative Memory from Memory Hierarchy. 10

## Section – II

10

5. Answers the following questions : (any  $5 \times 2$  marks each)

- (1) \_\_\_\_\_ is called Universal Gate.  
(a) NOT (b) AND  
(c) NAND (d) EX-OR
- (2) Full Adder require minimum Two Hal Adder. (True/False)
- (3) In \_\_\_\_\_ combinational circuit has  $n$  input lines and maximum  $2^n$  output line.  
(a) Decoder (b) Multiplexer  
(c) Encoder (d) Full Adder
- (4) Full form of RTL.
- (5) Convert  $456_{10}$  into 10's complement.
- (6) Operand is store in \_\_\_\_\_ part.  
(a) Accumulator (b) Memory Adders  
(c) Bus (d) All of the above
- (7) Cache Memory is fastest memory in computer system. (True/False)
- (8) DMA transfers are performed by \_\_\_\_\_ circuit.  
(a) Data Controller (b) Device Controller  
(c) DMA Controller (d) All of the above
- (9) Flip-flop store one bit of data. (True/False)
- (10) Bus system is used three state gates. (True/False)