

AL-107

April -2018

B.Sc., Sem.-II

CC-3, Paper-103 : Electronics

Time : 3 Hours]

[Max. Marks : 70

1. (a) Explain transistor as an amplifier. 7

OR

Discuss relation between α and β . And prove that $\alpha = \beta/(1+\beta)$. Draw the different transistor circuit configuration.

- (b) Draw the circuit of collector to base bias and obtain stability factor S. 7

OR

Draw the circuit of voltage divider bias and obtain stability factor S.

2. (a) Derive the expression for current gain, voltage gain, input resistance, output resistance and power gain of a transistor amplifier operating in the CE mode. 7

OR

Define the following parameters with their names :

- (i) h-parameters
(ii) Y-parameters
(iii) Z-parameters

- (b) Derive the general formula for voltage gain, current gain, input impedance and output impedance of a linear circuit in terms of h-parameter. 7

OR

Draw the circuit diagram of two stage R-C coupled amplifier. Derive an expression for the voltage gain in mid frequency region.

3. (a) Define series resonance, draw its complete circuit diagram and prove that $Z = R[1+jQ\delta(2 - \delta)]$ 7

OR

Derive the conversion formulas directly from impedance of π -network to T-network and T-network to π -network.

- (b) State and prove Maximum Power Transfer theorem. 7

OR

What is antiresonant ? Draw its circuit diagram and prove that

$$(1) f_{ar} = \frac{1}{2\pi} \sqrt{\frac{1}{LC}} \sqrt{1 - \frac{1}{Q^2}}$$

$$(2) X_L = X_C(1 - 1/Q^2)$$

$$(3) R_{ar} = L/CR$$

4. (a) Solve the Boolean expression $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D}$ by preparing truth table and thereby Karnaugh Map. Encircle all octets, quads, and pairs. 7

OR

What is BCD-TO-Decimal decoders? Draw a logic circuit diagram of a 1-of-10 decoder and explain its working with the help of 4-input logic levels.

- (b) Define demultiplexer. Draw the logic circuit diagram of a 1-to-16 demultiplexer, draw the pin diagram of its IC 74154 and prepare its truth table. 7

OR

Draw a logic diagram of a two-input exclusive OR gate using basic logic gates. Explain its working and give its symbol. Explain how to prepare four input Ex-OR gate from two input Ex-OR gate.

5. Answer in short : 14

- (1) Define stability in biasing circuit.
- (2) In which region transistor is heavily doped?
- (3) In which configuration amplifier has lowest voltage gain?
- (4) Which is the best method for biasing the transistor?
- (5) Draw the symbol of P- N- P and N- P- N transistor.
- (6) Which is the smallest of h- parameter of transistor.
- (7) Draw the seven-segment display.
- (8) Define the figure (factor) of merit, Q.
- (9) What is power factor?
- (10) What are Z_{1oc} , Z_{1sc} , Z_{2oc} and Z_{2sc} ?
- (11) What do you mean by don't care condition?
- (12) State D'Morgan's theorems.
- (13) Define bandwidth of a resonant circuit.
- (14) Give names of four basic method of coupling.