

DH-102

December-2018

B.Sc., Sem.-III

CC-201 : Electronics

Time : 2:30 Hours]

[Max. Marks : 70

Instructions : (1) All questions carry equal marks.

(2) Symbols have their usual meanings.

(3) Numbers on right side of questions indicate marks.

1. (A) (i) What is 'tilt' or 'sag' ? Draw the simplified low frequency model of CE amplifier for 'tilt' calculation. Discuss the low frequency response to a square wave and derive the formula for 'tilt'. 7
- (ii) Draw CE amplifier circuit and discuss the effect of coupling capacitor on low frequency response. 7
- OR**
- (i) Draw an approximate high frequency model for determination of the short circuit current gain. Derive the equation for CE short circuit current gain. 7
- (ii) Discuss the high frequency response of a transformer coupled amplifier. 7
- (B) Attempt any four : 4
- (1) Write Miller's theorem.
- (2) Write an equation for β cutoff frequency.
- (3) What is base spreading resistance ?
- (4) Write the reason for reduction of low frequency voltage gain of an amplifier.
- (5) What is transition capacitance ?
- (6) Write the formula for transistor transconductance gm.

2. (A) (i) Obtain an equation for voltage gain with feedback (A_{vf}) in terms of voltage gain without feedback (A_v) and feedback factor (K). 7
- (ii) Write types of negative feedback. Discuss the current series feedback in detail with suitable diagram. 7

OR

- (i) What do you understand by negative feedback? Write advantages of negative feedback and discuss any two advantages in detail with suitable diagram. 7
- (ii) (a) An amplifier's total harmonic distortion is reduced from 8% to 2% when 5% negative feedback is used. 7
- (1) What was the initial voltage gain of the amplifier when distortion was 8%?
- (2) What was the gain with 2% distortion?
- (b) An amplifier with $2.2 \text{ k}\Omega$ input resistance and $40 \text{ k}\Omega$ output resistance has a voltage gain of 80. The amplifier is now modified to provide 10% negative voltage feedback in series with the input. Calculate:
- (1) The voltage gain with feedback
- (2) The input resistance and output resistance with feedback.
- (B) Attempt any four: 4
- (1) Write disadvantage of negative feedback.
- (2) What type of negative feedback produce an increase in input resistance and decrease in output resistance?
- (3) A feedback amplifier essentially consists of an amplifier and _____ circuit.
- (4) Why negative feedback is called degerative?
- (5) Larger the feedback factor, higher or lower the gain stability of an amplifier.
- (6) With negative feedback upper 3dB frequency of an amplifier is increased or decreased.

3. (A) (i) Draw the FET family tree. Write advantages and disadvantages of the FET. 7
- (ii) Discuss the theory of operation of JFET for the following cases : 7
- (1) When $V_{gs} = 0$ & $V_{DS} = 0$ volt
- (2) When $V_{gs} = 0$ volt and V_{DS} is increased from zero
- (3) When $V_{DS} = 0$ volt and V_{gs} is increased from zero

OR

- (i) Draw the symbol for N channel DE MOSFET. Explain construction and working of DE MOSFET (Depletion MOSFET). 7
- (ii) Write short notes on FET as switch and FET applications. 7
- (B) Attempt any three : 3
- (1) What is FET ?
- (2) Draw the symbol of N channel JFET.
- (3) Why the name given MOSFET ?
- (4) Write the parameters of JFET.
- (5) Draw JFET drain characteristics with $V_{gs} = 0$ volt. Show Ohmic region and pinch off region.

4. (A) (i) Draw the circuit of shunt capacitor filter and explain circuit analysis for half wave rectifier. 7
- (ii) Draw the circuit of LC filter and CLC (pi filter) filter. Write comparison between them. 7

OR

- (i) Draw the circuit of Transistor series voltage regulator. Explain how this circuit provide load and line regulation. 7
- (ii) Draw the circuit of zener diode shunt regulator. Why this circuit is called shunt regulator ? Explain working of zener diode shunt regulator. 7

(B) Attempt any three :

- (1) Write the function of filter circuit.
 - (2) What is function of current regulator ?
 - (3) What is function of voltage regulator ?
 - (4) Write the advantage of Bleeder register.
 - (5) Draw the circuit of transistor shunt voltage regulator.
-