

NK-111

November-2017

B.Sc., Sem.- V

CC-301 : Electronics

Time : 3 Hours]

[Max. Marks : 70

1. Attempt any two :

14

- (A) Draw the circuit diagram of an emitter coupled differential amplifier, explain its working. Derive the equation for differential mode gain, common mode gain and CMRR.
- (B) Discuss about the transverse characteristic of an OPAMP.
- (C) Explain the method to improve CMRR of the differential amplifier by using constant current source.
- (D) Explain the working of the level shifting circuit in an OPAMP.

2. Attempt any two :

14

- (A) Draw the circuit of three input non-inverting summing amplifier using OPAMP. Derive the equation for output voltage.
- (B) Draw the circuit of a grounded load voltage to current converter using OPAMP. Explain its working.
- (C) Explain the use of OPAMP as an AC amplifier. Derive the equation of cut-off frequency.
- (D) Draw the circuit of full-wave rectifier using OPAMP and explain its working.

3. Attempt any two :

14

- (A) Discuss about regulator protection techniques.
- (B) Draw the functional block diagram of 3-terminal regulator. Explain its function how it can be used as fixed positive voltage regulator.
- (C) Draw the circuit diagram of 3-terminal adjustable voltage regulator. Explain its working and show that the total change in output voltage is $dV_o = S\Delta V_o + R_o\Delta I_o$.
- (D) Draw function block diagram of voltage regulator IC-723. Explain the use of IC-723 as positive low voltage regulator and derive the equation of output voltage.

4. Attempt any two :

14

- (A) Explain the different circuit schemes for switching regulators.
- (B) Draw the circuit diagram of basic buck type switching regulator and show that for this circuit output voltage is proportional to duty cycle of switching frequency.
- (C) For buck type switching regulator draw the waveform of switching voltage, inductor voltage, capacitor voltage and derive the equation for ripple voltage.
- (D) For buck type switching regulator derive the equation for minimum load current and critical inductance.

5. Answer the following in brief :

14

- (1) What is the function of the output stage in an OPAMP IC ?
 - (2) Define: Differential Mode Signal.
 - (3) Define : Common Mode Signal
 - (4) Why the name current mirror circuit is given ?
 - (5) Draw the circuit of a subtractor using OPAMP.
 - (6) What is the use of current to voltage converter circuit ?
 - (7) What is an instrumentation amplifier ?
 - (8) What is the advantage of OPAMP rectifier circuit over simple diode rectifier ?
 - (9) For what purpose voltage reference is used in IC regulators ?
 - (10) What is tracking regulator ?
 - (11) What is current regulator ?
 - (12) What is meant by switching regulator ?
 - (13) What is meant by boost type regulator ?
 - (14) Give full form of SMPS.
-