

## B.Sc. Sem-5 Examination

## CC 301

## Electronics

November 2021

Time : 2-00 Hours]

[Max. Marks : 50

- Instructions: (1) All questions in Section-I carry equal marks  
 (2) Attempt any Three questions in Section - I.  
 (3) Question - 1 in section - II is compulsory

SECTION - I

- Q-1 (A) Discuss about transfer characteristics of an Op-Amp. (7)  
 (B) Draw the circuit diagram of Emitter coupled differential amplifier along with its low frequency small signal equivalent circuit and derive the equation for closed loop voltage gain. (7)
- Q-2 (A) Explain the 'current mirror' method to improve CMRR of the differential amplifier. (7)  
 (B) In the basic differential amplifier circuit,  $R_C = 2 \text{ k}\Omega$ ;  $R_E = 4.3 \text{ k}\Omega$ ,  $V_{CC} = I_{V_{EE}} = 5 \text{ V}$ ;  $\beta_0 = 200$ ,  $V_{BE} = 0.7 \text{ V}$ . Determine the values of quiescent currents and voltages  $I_{BQ}$ ,  $I_{CQ}$ ,  $V_{O1}$ ,  $V_{O2}$ ,  $V_{CEQ}$  for both inputs  $V_1$  and  $V_2$  grounded. (7)
- Q-3 (A) Draw the circuit of a grounded load voltage to current converter using Op-Amp. Explain its working. (7)  
 (B) Explain with suitable diagram: Half-wave rectifier using Op-Amp. (7)
- Q-4 (A) Discuss in brief the application of Op-Amp as non-inverting summing amplifier. (7)  
 (B) Draw positive peak detector circuit using Op-Amp. Explain its working with suitable wave forms. (7)
- Q-5 (A) Draw the block diagram of series IC voltage regulator. Explain voltage reference block using Zener diode and how it is compensated by base-emitter diodes of transistors. (7)  
 (B) Write a short note on 3-Terminal positive IC voltage regulator. (7)
- Q-6 (A) Discuss about regulator protection techniques. (7)  
 (B) Discuss positive voltage regulator using IC  $\mu\text{A} 723$  using fold-back current limiting circuit. (7)
- Q-7 (A) Explain operation of switching regulator using LM 105. (7)  
 (B) For buck-type switching regulator, draw the waveform of switching voltage, inductor voltage, capacitor voltage and derive the equation for ripple voltage. (7)
- Q-8 (A) Explain the operation of free running switching regulator. (7)  
 (B) For buck-type switching regulator derive the equation for minimum load current and critical inductance. (7)

SECTION - II

- Q-9 Answer following in brief (Any Eight): (8)
- 1 What is virtual ground for Op-Amp?
  - 2 Full form of CMRR is \_\_\_\_\_.
  - 3 The CMRR is measured in \_\_\_\_\_ unit.
  - 4 Define: Common mode signal.
  - 5 Scale changer circuit using Op-Amp is also known as \_\_\_\_\_.
  - 6 \_\_\_\_\_ circuit is known as transconductance amplifier.
  - 7 What is instrumentation amplifier?
  - 8 What is the advantage of Op-Amp rectifier circuit over simple diode rectifier circuit?
  - 9 Write any one advantage of IC voltage regulator over discrete component regulator.
  - 10 Mention the purpose of 'voltage reference' used in IC regulators.
  - 11 What is the output voltage of regulator IC 7812?
  - 12 A 4-terminal IC regulator is superior to the 3-terminal IC regulator. Give reason.
  - 13 What is the purpose of switching mode operation in switching regulators?
  - 14 What is the full form of SMPS?
  - 15 LM 305 is \_\_\_\_\_ voltage regulator, whereas LM 304 is \_\_\_\_\_ voltage regulator.
  - 16 What is mean by boost type regulator?