

NE-106

November-2022

B.Sc., Sem.-V

304 : Physics

Time : 2½ Hours]

Max. Marks : 70

- સૂચનાઓ : (1) બધા જ પ્રશ્નો ફરજિયાત છે.
(2) સંજ્ઞાઓ તેમના પ્રચલિત અર્થ ધરાવે છે.
(3) જમણી બાજુના અંક પ્રશ્નના ગુણ દર્શાવે છે.

1. (A) આદર્શ એમ્પ્લિફાયરનો આઉટપુટ અવરોધ કેટલો હોવો જોઈએ ? જરૂરી સૂત્ર તથા પરિપથની મદદથી તે સમજાવો. એમ્પ્લિફાયરનો આઉટપુટ અવરોધ કેવી રીતે નક્કી કરી શકાય ? 7

અથવા

હાર્મોનિક ડિસ્ટોર્શન (harmonic distortion) એટલે શું ? એમ્પ્લિફાયર માટે હાર્મોનિક ડિસ્ટોર્શન માપવાની ત્રણ બિંદુ (Three points) રીતનું વર્ણન કરો અને A_0 , A_1 તથા A_2 કંપવિસ્તાર મેળવો. 7

- (B) ડેસીબેલ શું છે ? શૂન્ય ડેસીબેલ સંદર્ભ લેવલ સમજાવો. ડેસીબેલની લાક્ષણિકતાઓ આપો. નીચે મુજબ સમીકરણ

$$dB = 20 \log \left(\frac{V_o}{V_i} \right) + 10 \log \left(\frac{R_i}{R_o} \right) \text{ તારવો. } 7$$

અથવા

વોલ્ટમીટરના ડેસીબેલ મીટર તરીકે ઉપયોગ વિશે સવિસ્તાર સમજાવો. 7

2. (A) યુક્તિ કરેલ CE વિવર્ધકના ત્રણ વિભાગો (cascaded three stages)ની સ્વચ્છ આકૃતિ દોરો અને વોલ્ટેજ ગેઈનનું સૂત્ર મેળવો. 7

અથવા

CE એમ્પ્લિફાયરના નિમ્ન આવૃત્તિ (low frequency) રીસ્પોન્સ પર એમીટર બાયપાસ કેપેસિટરની અસર સમજાવો. 7

- (B) હાઈબ્રીડ π કેપેસિટન્સ (hybrid π capacitance), બેઝ સ્પ્રેડીંગ અવરોધ અને ટ્રાન્ઝીસ્ટર ટ્રાન્સકંડક્ટન્સ વિશે સમજૂતી આપો. 7

અથવા

સ્ક્વેર વેવ (square wave) માટે એમ્પ્લિફાયરના ઉચ્ચ આવૃત્તિ રિસ્પોન્સની ચર્ચા કરો. 7

3. (A) બે ઈનપુટ ધરાવતાં EX-OR ગેટની વિસ્તૃત સમજૂતી આપો. ત્રણ ઈનપુટ અને ચાર ઈનપુટ ધરાવતાં EX-OR ગેટના માત્ર પરિપથ ડાયગ્રામ દોરો. 7

અથવા

મીનીટર્મ (mini term) વડે દર્શાવેલ લોજિક સમીકરણ $y = \sum m(0, 1, 4, 5, 11, 14, 15)$ માટેનું કાર્નુમેપનો ઉપયોગ કરી સરળ બુલિયન સમીકરણ તારવો. આનુષંગિક સમ ઓફ પ્રોડક્ટ લોજિક પરિપથ દોરો : 7

- (i) OR અને AND જેવા મૂળભૂત ગેટનો ઉપયોગ કરી.
(ii) માત્ર NAND ગેટનો ઉપયોગ કરી.

- (B) RS ફ્લીપ-ફ્લોપ (flip-flop)ની વિસ્તૃત સમજૂતી આપો. 7

અથવા

JK ફ્લીપ-ફ્લોપ (flip-flop) વિશે નોંધ લખો. 7

4. (A) T-જાળતંત્ર અને π -જાળતંત્ર (network) માટે અરસ-પરસ સમતુલ્ય જાળતંત્રમાં રૂપાંતરણની રીત જરૂરી સૂત્રો તારવીને સમજાવો. 7

અથવા

“મહત્તમ પાવર ટ્રાન્સફર” પ્રમેય લખો અને સાબિત કરો. 7

- (B) અવબાધ (impedance),

$Z = R + j\left(\omega L - \frac{1}{\omega C}\right)$ નો ઉપયોગ કરી શ્રેણી અનુનાદ પરિપથમાં અનુનાદ આવૃત્તિથી નાના

વિચલન માટે જરૂરી અવબાધ (impedance) $Z = R \{1 + jQ\delta(2 - \delta)\}$ નું સમીકરણ તારવો. 7

અથવા

સમાંતર અનુનાદ પરિપથનું વિસ્તૃત વર્ણન કરો. f_{ar} નું સમીકરણ તારવો અને $R_{ar} = \frac{L}{CR}$ મેળવો. 7

5. ગમે તે સાત પ્રશ્નોના જવાબ આપો (દરેક પ્રશ્નના ગુણ બે છે) :

14

- (1) એક એમ્પ્લિફાયરના સિમ્લ ઈનપુટ વોલ્ટેજ $V_i = 0.25 \text{ V}$ છે અને તે ઉદ્ગમમાંથી 1 mA પ્રવાહ મેળવે છે. એમ્પ્લિફાયર 10 mA પ્રવાહ ઉદ્ભારને 10 V આપે છે તો પ્રવાહ ગેઈન, વોલ્ટેજ ગેઈન અને પાવર ગેઈન મેળવો.
- (2) પાંચ પોઈન્ટ (five point) પદ્ધતિમાં જુદા-જુદા હાર્મોનિક ડિસ્ટોર્શન (harmonic distortion) અનુક્રમે $D_2 = 3.26\%$, $D_3 = 2.17\%$ અને $D_4 = 1.04\%$ હોય તો કુલ હાર્મોનિક ડિસ્ટોર્શન D શોધો.
- (3) એક એમ્પ્લિફાયરનો પાવર ગેઈન 30 dB મળે છે. જો આઉટપુટ પાવર 6 વૉટ (watt) હોય તો ઈનપુટ પાવરની ગણતરી કરો.
- (4) 10% થી વધારે સેગ (sag) ન હોય તેવી 100 Hz સ્ક્વેર તરંગ (square wave) મેળવવા માટે નિમ્ન 3 dB આવૃત્તિ (lower 3 dB frequency)ની ગણતરી કરો.
- (5) શા માટે કાસ્કેડ (cascaded) એમ્પ્લિફાયરનો કુલ વોલ્ટેજ ગેઈન બધા જ સ્ટેજના વોલ્ટેજ ગેઈનના ગુણાકાર બરાબર હોય છે પરંતુ કુલ પ્રવાહ ગેઈન બધા જ સ્ટેજના પ્રવાહ ગેઈનના ગુણાકાર બરાબર હોતો નથી ?
- (6) CE એમ્પ્લિફાયરના કાસ્કેડ જોડાણની રીતના નામ આપો.
- (7) ડીમોર્ગન પ્રમેયના કથન લખો.
- (8) નીચે આપેલ બુલિયન સમીકરણ


$Y = (\bar{A} + B)(A + B)$ માટેનું લોજિક પરિપથ દોરો. બુલિયન ગણિત (algebra)નો ઉપયોગ કરી શક્ય સાદું લોજિક પરિપથ દોરો.

(9) કાર્નુમેપ (Karnaugh map) શું છે ? ચાર ચલ માટે કાર્નુમેપમાં કેટલી એન્ટ્રી હશે ?

(10) π નેટવર્કમાં $Z_A = Z_B = Z_C = 6 \Omega$ હોય તો T સમતુલ્ય નેટવર્ક શોધો.

(11) T નેટવર્કમાં $Z_1 = Z_2 = Z_3 = 4 \Omega$ હોય તો π -સમતુલ્ય નેટવર્ક શોધો.

(12) આપેલ T-નેટવર્ક પરિપથ

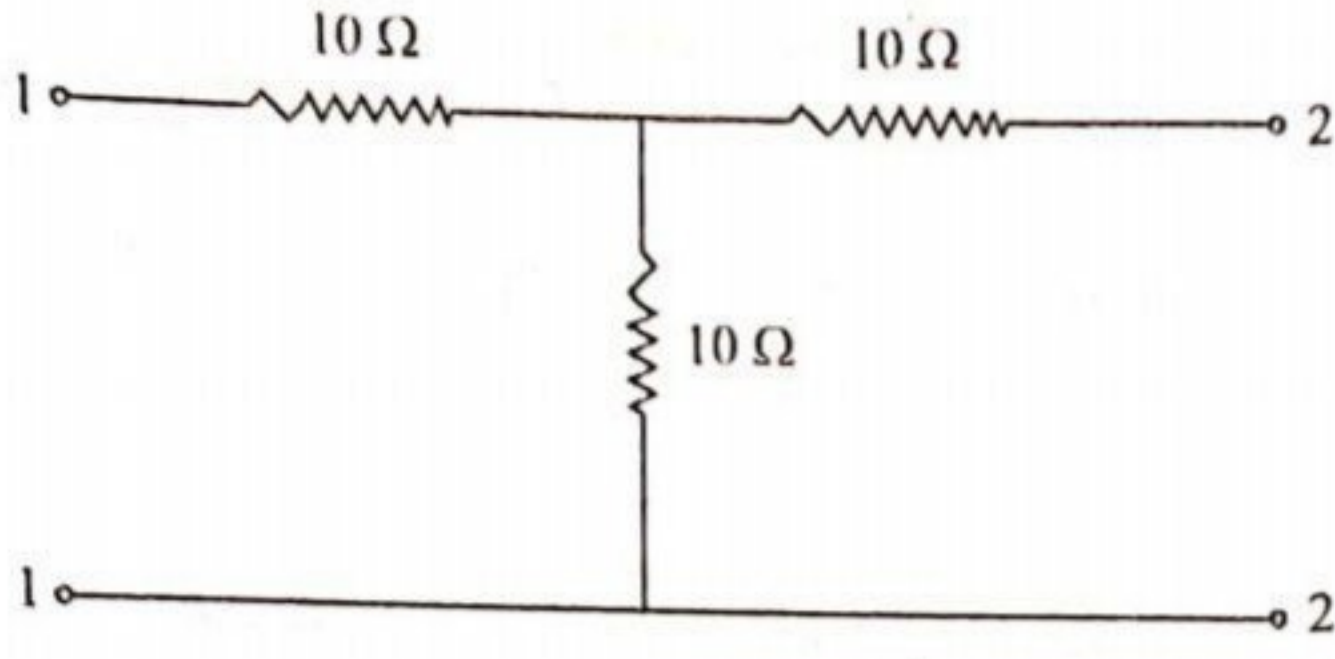

માટે Z_{10c} અને Z_{1Sc} શોધો.

@geniusguraji

NE-106

November-2022

B.Sc., Sem.-V

304 : Physics

Time : 2½ Hours]

[Max. Marks : 70

- Instructions :
- (1) All questions are compulsory.
 - (2) The symbols have their usual meaning.
 - (3) Figures on the Right Hand Side show marks.

1. (A) What would be the output resistance of an ideal amplifier ? Explain it with necessary formula and circuit. How one can determine output resistance of an amplifier ?

7

OR

What is harmonic distortion ? Explain three points method of calculating harmonic distortion for amplifier. Obtain amplitude A_0 , A_1 and A_2 .

7

- (B) What is Decibel ? Explain zero decibel reference level. Give characteristics of decibel. Derive $\text{dB} = 20 \log \left(\frac{V_o}{V_i} \right) + 10 \log \left(\frac{R_i}{R_o} \right)$.

7

OR

Explain how voltmeter can be used as a decibel indicator in detail.

7

2. (A) Draw neat circuit diagram of three cascaded stages of CE amplifier and derive the equation for voltage gain.

7

OR

Explain the effect of emitter bypass capacitor on low frequency response of CE amplifier.

7

- (B) Explain about hybrid π capacitance, base spreading resistance and transistor transconductance. 7

OR

Describe amplifier's high frequency response to a square wave. 7

3. (A) Explain two input EX-OR gate in detail. Draw only circuit diagram of three input and four input EX-OR gate. 7

OR

Derive simplified Boolean equation using Karnaugh map for the logic equation expressed in mini terms $y = \Sigma m(0, 1, 4, 5, 11, 14, 15)$: 7

Draw the corresponding sum of product logic circuit:

(i) Using basic logic gates (OR and AND)

(ii) Using only NAND gate

- (B) Explain in detail RS flip-flop. 7

OR

Write a note on JK flip-flop. 7

4. (A) Explain the method to convert a T-network into equivalent π network and vice-versa by deriving necessary formula. 7

OR

State and prove "Maximum Power Transfer" theorem. 7

- (B) Using the impedance, $Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$ of the series resonance circuit, derive the equation for impedance $Z = R \{ 1 + jQ\delta(2 - \delta) \}$ for small deviations from the resonant frequency. 7

OR

Describe parallel resonance circuit in detail. Derive equation of f_{ar} and obtain

$$R_{ar} = \frac{L}{CR}$$

5. Answer any **seven** questions : (Each question of 2 marks) :

14

- (1) An amplifier has a signal input voltage V_i of 0.25 V and draws 1 mA current from the source. The amplifier delivers 10 V to a load at 10 mA. Determine the current gain, voltage gain and power gain.
- (2) In a five point method, different harmonic distortions are $D_2 = 3.26\%$, $D_3 = 2.17\%$ and $D_4 = 1.04\%$ respectively. Find total harmonic distortion D.
- (3) The power gain of an amplifier is obtained 30 dB. If the output power is 6 watt, calculate the input power.
- (4) Calculate the lower 3 dB frequency to reproduce 100 Hz square wave with not more than 10% sag.
- (5) Why is it that the total voltage gain of a cascaded amplifier is the product of all the stage voltage gain, but the total current gain is not the product of all the stage current gain ?
- (6) Name the methods to cascade CE amplifier.
- (7) Write the statement of De-Morgan's theorem.
- (8) Draw the logic circuit for Boolean equation :

$$Y = (\bar{A} + B)(A + B)$$

Draw Simplified logic circuit as much as possible using Boolean algebra.


- (9) What is Karnaugh map ? How many entries are there on a four variables Karnaugh map ?

(10) In a π network $Z_A = Z_B = Z_C = 6 \Omega$. Find T equivalent network.

(11) In T-network $Z_1 = Z_2 = Z_3 = 4 \Omega$. Find equivalent π -network.

P.T.O.

(12) For a given T-network

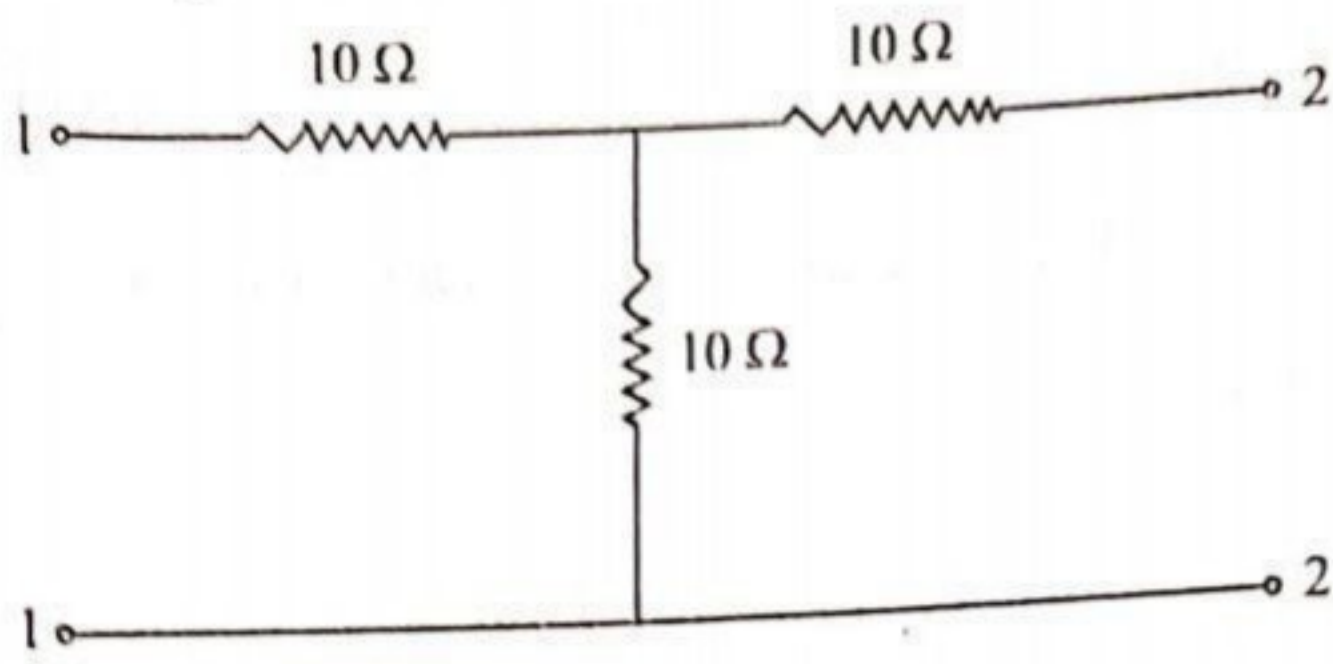

Find the value of Z_{1Oc} and Z_{1Sc} .

@geniusguruzi